

# **Signed 8-bit Pocket Calculator Project with fundamental operations**


## **Table of Contents:**

1. General Statement
2. Basic Functioning Procedure
3. General Block Diagram
4. Component Block Diagram
5. General State Diagram
6. Execution Unit Description
7. Control Unit Description

## Statement:

**A10)** Să se proiecteze un **calculator de buzunar cu operații aritmetice fundamentale** (adunare, scădere, înmulțire, împărțire). Operațiile de înmulțire și împărțire se vor implementa folosind algoritmi specifici, nu operatorii limbajului. Operanzii sunt reprezentați pe 8 biți cu semn. Operanzii și operatorii vor fi introduși secvențial în formă zecimală. Se vor folosi afișajele cu 7 segmente de pe plăcuțele cu FPGA. Proiectul va fi realizat de **1 student**.

## Basic Functioning Procedure:

 

Considering each half of the switch array as an 8-bit signed number, the user can input two numbers in two's complement on eight bits. The input numbers, before

an operation is selected, are shown on each half of the seven segment display.

The syntax is as follows :

$$\text{No1 OP No2} = \text{Result}$$

The buttons' meaning is as follows :


	Addition	
Multiplication	Reset	Division
	Subtraction	

Top = Addition, Bottom = Subtraction, Left = Multiplication, Right = Subtraction, Middle = Reset ( goes back to the two-number displaying and selecting).

After pressing any operation button, the calculator will display the selected operation's result on the seven-segment display, as a single number.

Example usage:

Say the user inputs these two numbers:

 


(intended max ranges showcase for 8-bit 2's complement representation)

And then decides to call the "multiply" operation. After the execution of the operation the seven-segment display will look like this:




After this number is displayed, the calculator will await the 'reset' input from the user. After that selection, the calculator goes back to the number selecting scheme.


## General block diagram:

 

## Component block diagram:

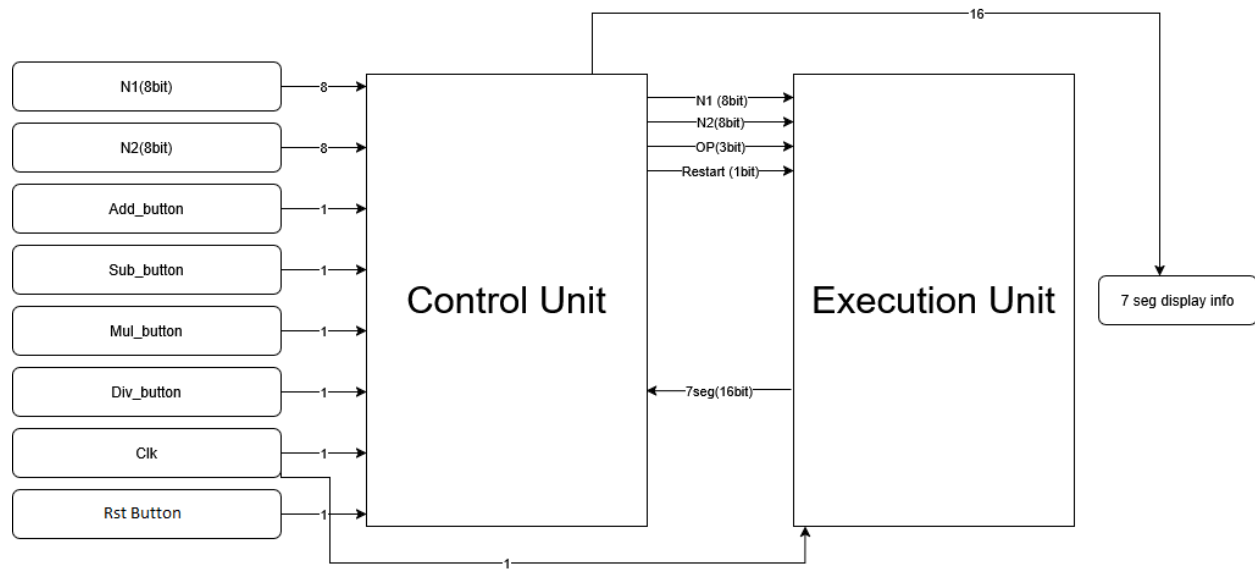

## State Diagram:

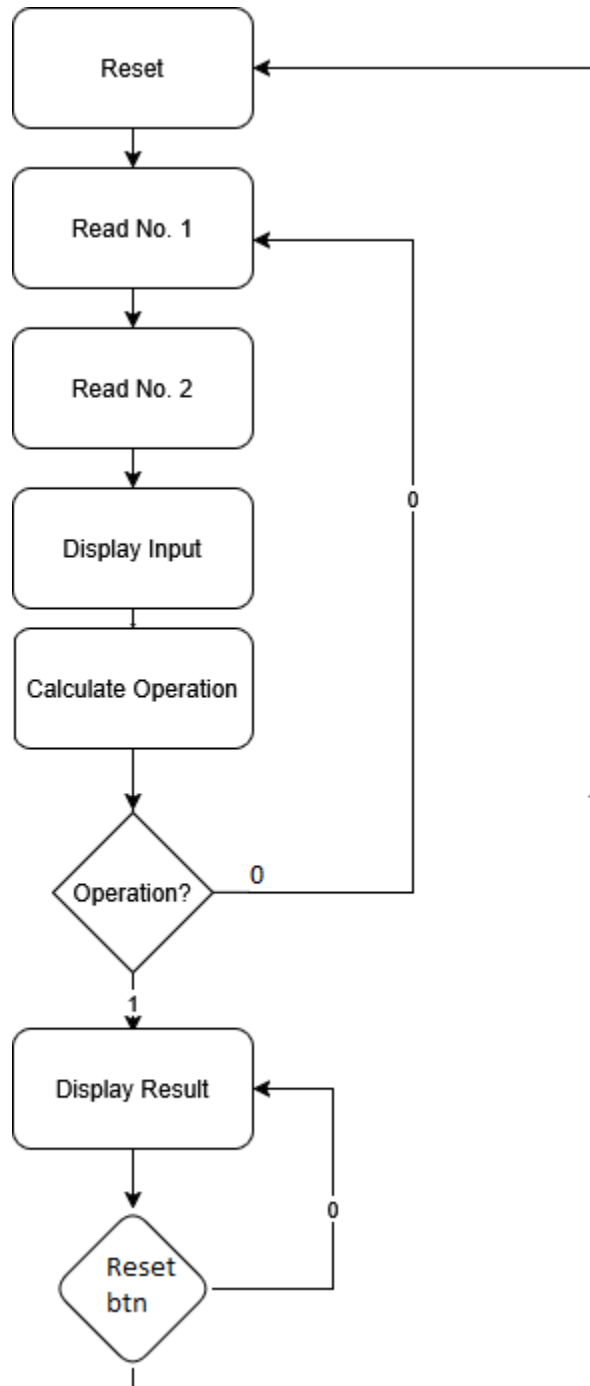

## Execution Unit

In the following pages I will proceed to describe the following components:

1. Data register 8-bit
2. Arithmetic logic unit
  - a. Mux 2 to 1 on 64bits
  - b. Mux 4 to 1 on 64bits
  - c. Mux 8 to 1 on 64bits
  - d. Adder unit
    - i. Full Adder 1-bit
    - ii. Full Adder 8-bit
    - iii. General structure
  - e. Subtractor unit
    - i. Full Subtractor 1-bit
    - ii. Full Adder 8-bit
    - iii. General structure
  - f. Multiplier Unit
    - i. State Diagram
  - g. Division Unit
    - i. State Diagram



- h. Output processors
  - i. Addition
  - ii. Subtraction
  - iii. Multiplication
  - iv. Division
- i. ALU General Structure
- 3. Display Unit
  - a. Eight-bit two's complement to seven segment display ROM
  - b. Three-bit counter with clock divider
  - c. Seven-segment displayer
    - i. Three-bit decoder
    - ii. 8 to 1 Mux on 8bits
    - iii. General structure
  - d. Display Unit general structure
- 4. Execution Unit General Structure

## 1. Data register 8 bit

Purpose :

1. To secure no feedback loops are asynchronous (VHDL Bitstream Error)
2. To hold data for the other components in the Execution Unit

Inputs :


1. Load\_inp : the 8 bits that are loaded onto the register
2. Load : the decision bit, active on '1'
3. Clk : Clock
4. Rst : clears the information stored


Outputs:

1. Outp: The information stored inside the register

Logic Scheme (on next page)

Black box:

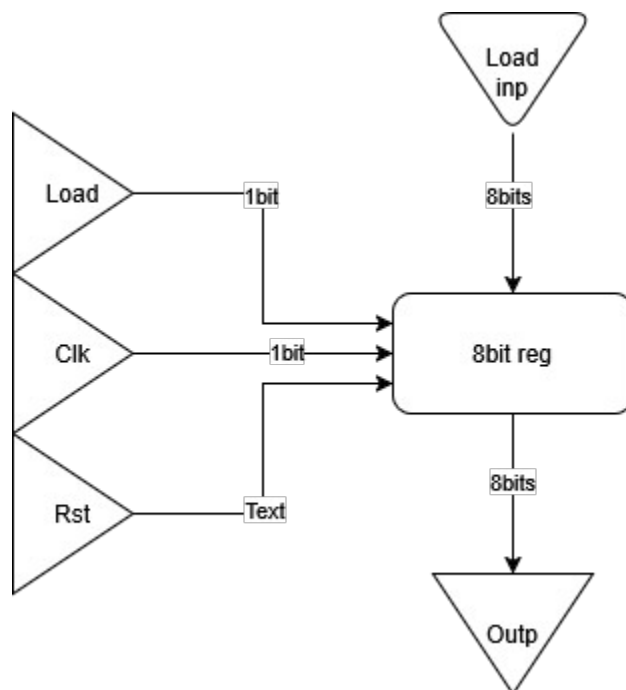

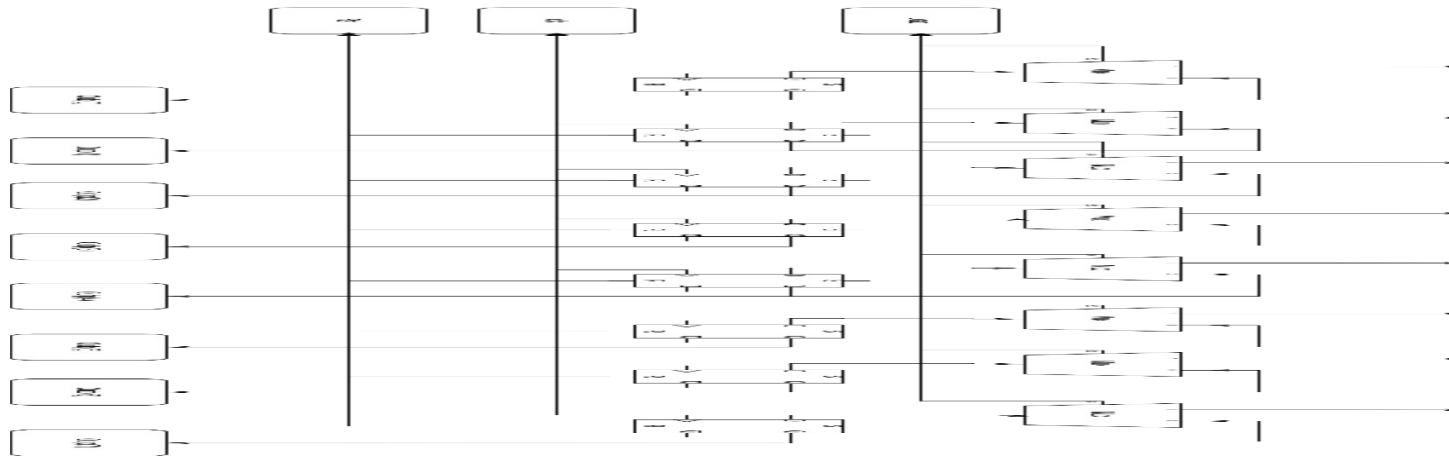

Vhdl Code:

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity data_register_8_bit is
4     Port ( Load : in STD_LOGIC;
5           Clk : in STD_LOGIC;
6           Rst : in STD_LOGIC;
7           Load_inp : in STD_LOGIC_VECTOR (7 downto 0);
8           Outp : out STD_LOGIC_VECTOR (7 downto 0));
9 end data_register_8_bit;
10
11 architecture Behavioral of data_register_8_bit is
12
13     signal info : std_logic_vector ( 7 downto 0) := x"00";
14
15     begin
16
17     Outp <= info;
18
19     process (Load,Clk,Rst)
20     begin
21         if rising_edge(clk) then
22             if Rst = '1' then
23                 info <= x"00";
24             elsif Load = '1' then
25                 info <= Load_inp;
26             else
27                 info <= info;
28             end if;
29         end if;
30     end process;
31
32 end Behavioral;
33
```

## 2.Arithmetic Logic Unit

### a. 2 to 1 Mux on 64 bits

Purpose : To pick between two 64bit options


Inputs :

1. In1 : 64 bits, first option
2. In2 : 64 bits, second option
3. S : selection bit


Outputs:

1. Outp : 64 bits, selected option

Logic scheme:

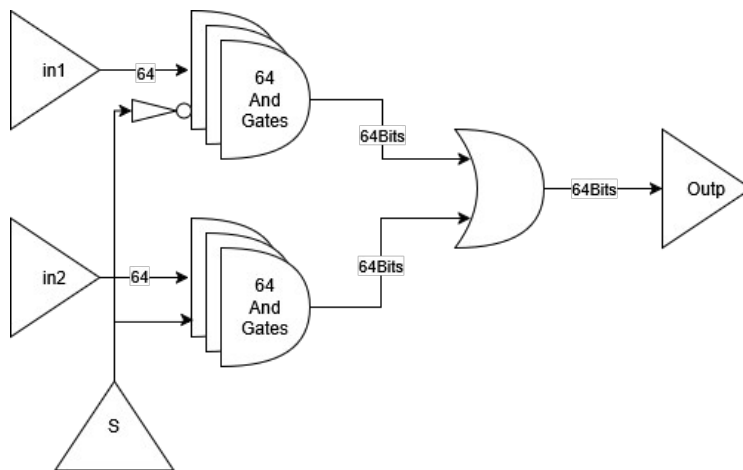

Black Box:

 

VHDL Code:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  entity mux_2tol_64bits is
5      Port ( in1 : in STD_LOGIC_VECTOR (63 downto 0);
6            in2 : in STD_LOGIC_VECTOR (63 downto 0);
7            s  : in STD_LOGIC;
8            outp : out STD_LOGIC_VECTOR (63 downto 0));
9  end mux_2tol_64bits;
10
11 architecture Behavioral of mux_2tol_64bits is
12
13 begin
14
15     outp <= in1 when s = '0' else in2;
16
17 end Behavioral;
18
```

## b.4 to 1 mux on 64 bits

Purpose: To pick between 4 options on 64 bits


Inputs:

1. In1, in2 , in3, in4 : 64 bits option bitstrings
2. S : 2 bit selection bitstring


Outputs

1. Outp : 64 bit selected bitstring

Logic scheme:

 

Black Box:

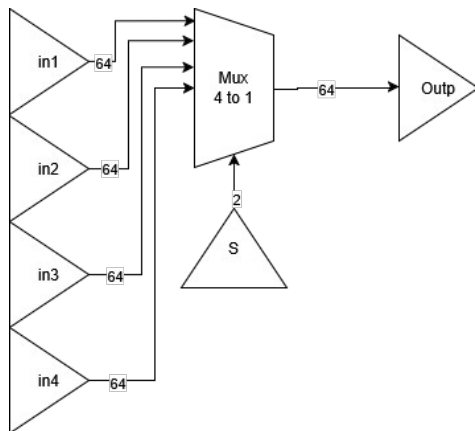

## Vhdl Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity mux_4tol_64bits is
    Port (
        in1 : in std_logic_vector(63 downto 0);
        in2 : in std_logic_vector(63 downto 0);
        in3 : in std_logic_vector(63 downto 0);
        in4 : in std_logic_vector(63 downto 0);
        s : in std_logic_vector(1 downto 0);
        outp : out STD_LOGIC_VECTOR (63 downto 0)
    );
end mux_4tol_64bits;

architecture Behavioral of mux_4tol_64bits is

    component mux_2tol_64bits is
        Port ( in1 : in STD_LOGIC_VECTOR (63 downto 0);
              in2 : in STD_LOGIC_VECTOR (63 downto 0);
              s : in STD_LOGIC;
              outp : out STD_LOGIC_VECTOR (63 downto 0));
    end component mux_2tol_64bits;

    signal outp_mux1 : std_logic_vector ( 63 downto 0);
    signal outp_mux2 : std_logic_vector ( 63 downto 0);

begin

    c0: mux_2tol_64bits port map ( in1 => in1, in2 => in2, s => s(0), outp => outp_mux1);
    c1: mux_2tol_64bits port map ( in1 => in3, in2 => in4, s => s(0), outp => outp_mux2);
    c2: mux_2tol_64bits port map ( in1 => outp_mux1, in2 => outp_mux2, s=>s(1), outp=>outp);
end Behavioral;
```



## c.8 to 1 mux on 64 bits

Purpose:

To pick between 8 selections

Inputs :


1. In1,in2, in3,in4,in5,in6,in7,in8 : selection 64-bit bitstrings
2. S : 3 bit bitstring


Outputs:

1. Outp : 64 -bit bitstring that has been selected by mux

Logic Scheme(on next page):

Black box:

 

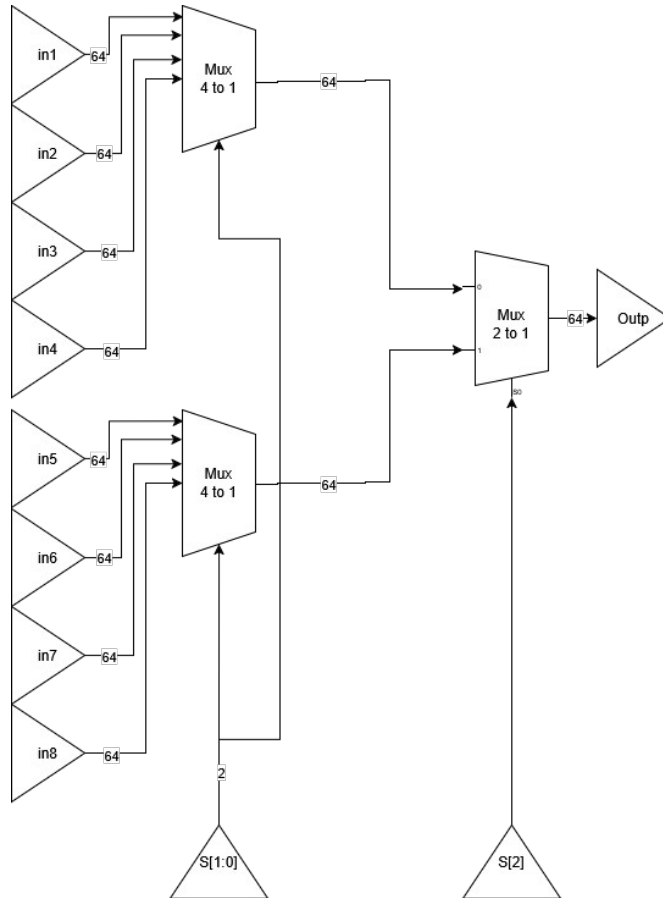

Vhdl Code:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  entity mux_8tol_64bits is
4  Port ( in1 : in std_logic_vector(63 downto 0);
5         in2 : in std_logic_vector(63 downto 0);
6         in3 : in std_logic_vector(63 downto 0);
7         in4 : in std_logic_vector(63 downto 0);
8         in5 : in std_logic_vector(63 downto 0);
9         in6 : in std_logic_vector(63 downto 0);
10        in7 : in std_logic_vector(63 downto 0);
11        in8 : in std_logic_vector(63 downto 0);
12        s : in std_logic_vector(2 downto 0);
13        outp : out STD_LOGIC_VECTOR (63 downto 0)
14        );
15  end mux_8tol_64bits;
16  architecture Behavioral of mux_8tol_64bits is

```

```
17 component mux_4tol_64bits is
18   Port (
19     in1 : in std_logic_vector(63 downto 0);
20     in2 : in std_logic_vector(63 downto 0);
21     in3 : in std_logic_vector(63 downto 0);
22     in4 : in std_logic_vector(63 downto 0);
23     s : in std_logic_vector(1 downto 0);
24     outp : out STD_LOGIC_VECTOR (63 downto 0)
25   );
26 end component mux_4tol_64bits;
27 component mux_2tol_64bits is
28   Port ( in1 : in STD_LOGIC_VECTOR (63 downto 0);
29         in2 : in STD_LOGIC_VECTOR (63 downto 0);
30         s : in STD_LOGIC;
31         outp : out STD_LOGIC_VECTOR (63 downto 0));
32 end component mux_2tol_64bits;
33 signal outp_mux1 : std_logic_vector ( 63 downto 0);
34 signal outp_mux2 : std_logic_vector ( 63 downto 0);
35 begin
36 c0: mux_4tol_64bits port map ( in1 => in1, in2=> in2, in3=>in3, in4=>in4,
37                               s => s(1 downto 0), outp => outp_mux1);
38 c1: mux_4tol_64bits port map ( in1 => in5, in2=> in6, in3=>in7, in4=>in8,
39                               s => s(1 downto 0), outp => outp_mux2);
40 c2: mux_2tol_64bits port map ( in1 => outp_mux1, in2 => outp_mux2, s=>s(2), outp=>outp);
41 end Behavioral;
42
```

## d.Adder Unit

### i.1-bit full Adder

Purpose:

To calculate the sum and carry-out of two bits and a carry-in.


Inputs:

1. a: first input bit
2. b: second input bit
3. Cin: carry-in bit


Outputs:

1. Cout : carry-out bit
2. S : sum bit

Logic Scheme:

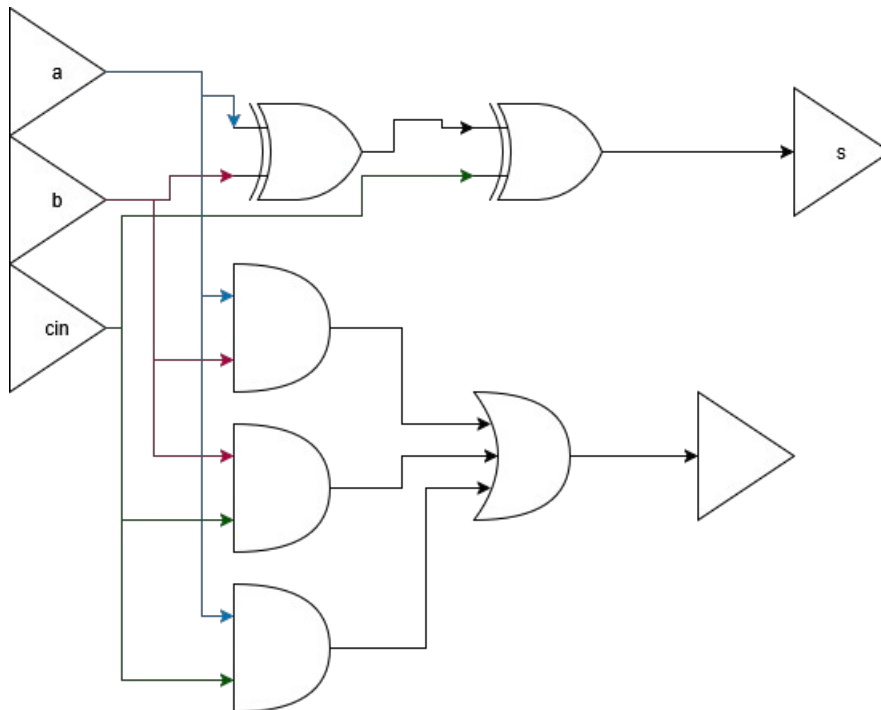

Black Box:

 

Vhdl Code:

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity full_adder_lbit is
5     Port ( a : in STD_LOGIC;
6           b : in STD_LOGIC;
7           Cin : in STD_LOGIC;
8           Cout : out STD_LOGIC;
9           S : out STD_LOGIC);
10 end full_adder_lbit;
11
12 architecture Behavioral of full_adder_lbit is
13
14 begin
15
16     S <= a xor b xor Cin;
17     Cout <= (a and b) or (a and Cin) or (b and Cin);
18
19 end Behavioral;
20
```

## ii.8-bit full adder

Purpose:

To calculate the sum of two 8bit numbers


Inputs:

1. A: 8bit input
2. B: 8bit input
3. Cin: carry-in input


Outputs:

1. Cout: carry-out output
2. S: The sum of A and B and Carry-in on 8 bits

Logic Scheme:

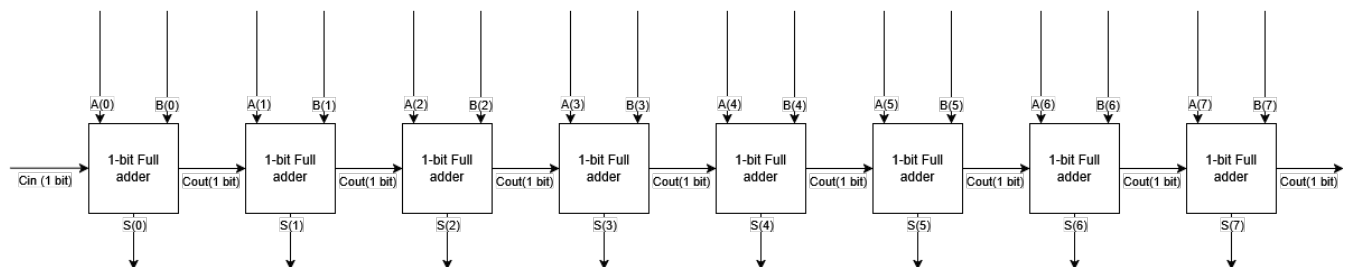

Black box:

 

## Vhdl Code:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  entity full_adder_8bit is
4      Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
5            B : in STD_LOGIC_VECTOR (7 downto 0);
6            Cin : in STD_LOGIC;
7            Cout : out STD_LOGIC;
8            S : out STD_LOGIC_VECTOR (7 downto 0));
9  end full_adder_8bit;
10 architecture Behavioral of full_adder_8bit is
11     component full_adder_1bit is
12         Port ( a : in STD_LOGIC;
13               b : in STD_LOGIC;
14               Cin : in STD_LOGIC;
15               Cout : out STD_LOGIC;
16               S : out STD_LOGIC);
17     end component full_adder_1bit;
18     signal inside_carries : std_logic_vector (8 downto 0);
19     begin
20         inside_carries(0) <= Cin;
21         adders: for i in 0 to 7 generate
22             adder: full_adder_1bit port map ( a => A(i), b => B(i),
23                                               cin => inside_carries(i), cout => inside_carries(i+1),
24                                               S => S(i));
25         end generate;
26         Cout <= inside_carries(8);
27     end Behavioral;
```

### iii. Adder-unit general structure

Purpose:

To calculate the sum of two eight bit numbers. Because the result can be a 2's complement number on 9 bits, the two inputs have to be resized before calculating their sum.


Inputs :

1. A : 8 bit number in 2's complement
2. B : 8bit number in 2's complement

Outputs:


1. S : 9 bit number in 2's complement

Logic Scheme:

 



Black Box:

 

Vhdl Code:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  entity adder_unit is
5      Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
6            B : in STD_LOGIC_VECTOR (7 downto 0);
7            S : out STD_LOGIC_VECTOR (8 downto 0)
8          );
9  end adder_unit;
10 architecture Behavioral of adder_unit is
11     component full_adder_8bit is
12         Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
13               B : in STD_LOGIC_VECTOR (7 downto 0);
14               Cin : in STD_LOGIC;
15               Cout : out STD_LOGIC;
16               S : out STD_LOGIC_VECTOR (7 downto 0));
17     end component full_adder_8bit;
18     component full_adder_lbit is
19         Port ( a : in STD_LOGIC;b : in STD_LOGIC;
20               Cin : in STD_LOGIC;Cout : out STD_LOGIC;
21               S : out STD_LOGIC);
22     end component full_adder_lbit;
23     signal extended_a : std_logic_vector ( 8 downto 0);
24     signal extended_b : std_logic_vector ( 8 downto 0);
25     signal internal_carry : std_logic;
26     begin
27     extended_a <= std_logic_vector(resize(signed(A), 9));
28     extended_b <= std_logic_vector(resize(signed(B), 9));
29     c0: full_adder_8bit port map ( A => extended_a (7 downto 0), B => extended_b (7 downto 0),
30                                   Cin=> '0',Cout => internal_carry,S => S(7 downto 0));
31     c1: full_adder_lbit port map ( a => extended_a (8),b => extended_b (8),
32                                   Cin=> internal_carry,Cout => open, S => S(8));
33     end Behavioral;
34
```

Didn't describe the logic behind the resizer because it's just a command in VHDL.

## e.Subtractor Unit

### i. 1-bit full Subtractor

Purpose:

To calculate the difference between two one-bit numbers


Inputs:

1. A : first 1bit number
2. B: second 1bit number
3. Bin : borrow-in bit


Outputs:

1. Bout: borrow-out bit
2. D: difference bit

Logic scheme:

 

Black box:

 

Code:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  entity full_subtractor_lbit is
4      Port ( a : in STD_LOGIC;
5            b : in STD_LOGIC;
6            bin : in STD_LOGIC;
7            bout : out STD_LOGIC;
8            d : out STD_LOGIC);
9  end full_subtractor_lbit;
10 architecture Behavioral of full_subtractor_lbit is
11 begin
12     d <= a xor b xor bin;
13     bout <= (not (a xor b) and bin) or (not a and b);
14 end Behavioral;
```

## ii. 8bit Full subtracter

Purpose:

To calculate the difference between two eight-bit numbers.


Inputs:

4. A : first 8bit number
5. B: second 8bit number
6. Bin : borrow-in bit


Outputs:

3. Bout: borrow-out bit
4. D: difference 8-bit number

Logic scheme:

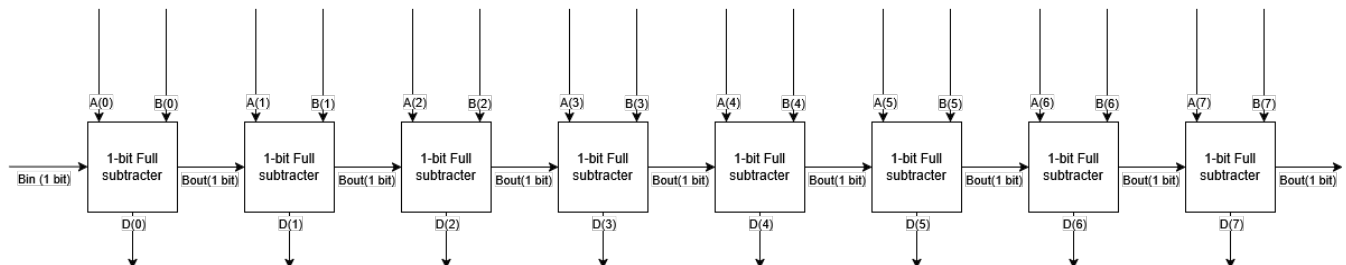

Black box:

 

### **iii.Subtraction Unit General Structure**

Purpose:

To calculate the difference of two eight bit numbers. Because the result can be a 2's complement number on 9 bits, the two inputs have to be resized before calculating their difference.


Inputs :

3. A : 8 bit number in 2's complement
4. B : 8bit number in 2's complement


Outputs:

2. D : 9 bit number in 2's complement

Logic Scheme:

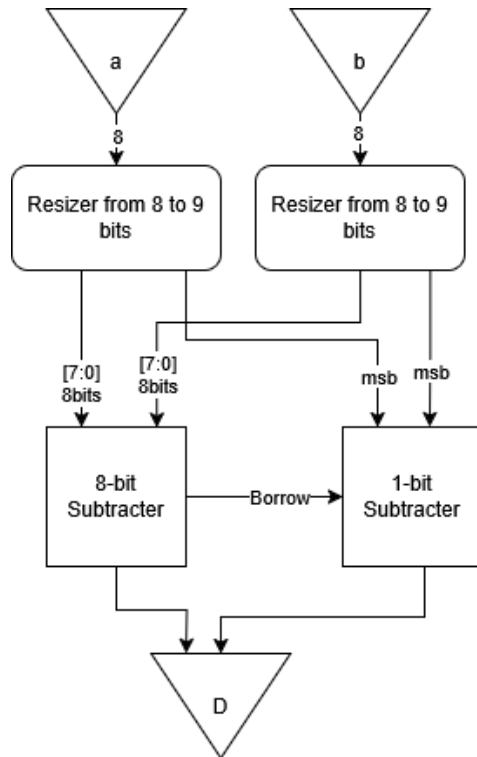

Black Box:

 

Vhdl Code:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  entity full_subtractor_8bit is
4      Port ( a : in STD_LOGIC_VECTOR (7 downto 0);
5            b : in STD_LOGIC_VECTOR (7 downto 0);
6            bin : in STD_LOGIC;
7            bout : out STD_LOGIC;
8            d : out STD_LOGIC_VECTOR (7 downto 0));
9  end full_subtractor_8bit;
10 architecture Behavioral of full_subtractor_8bit is
11     component full_subtractor_lbit is
12         Port ( a : in STD_LOGIC;
13               b : in STD_LOGIC;
14               bin : in STD_LOGIC;
15               bout : out STD_LOGIC;
16               d : out STD_LOGIC);
17     end component full_subtractor_lbit;
18     signal inside_borrows : std_logic_vector (8 downto 0);
19     begin
20         inside_borrows(0) <= bin;
21         borrows: for i in 0 to 7 generate
22             borrow: full_subtractor_lbit port map ( a => a(i), b=> b(i),
23                                                       bin => inside_borrows(i),
24                                                       bout=> inside_borrows(i+1),
25                                                       d => d(i));
26         end generate;
27         bout <= inside_borrows(8);
28     end Behavioral;
29 
```

## f.Multiplier Unit

### i.State Diagram


Main Reasoning behind the Multiplication algorithm:

Shift and add:

$$\begin{aligned}\text{Example : } 1010 * 1100 &= (1000 + 0010) * 1100 = 1000 * 1100 + 0010 * 1100 = \\ &= 1100 \ll 3 + 1100 \ll 1 = \\ &= 1100 \ll 3 * N_{1_3} + 1100 \ll 2 * N_{1_2} + 1100 \ll 1 * N_{1_1} + 1100 * N_{1_0}\end{aligned}$$

Based on the bits of the first number, we can determine what shifted versions of the second we can add to the sum. The pro of this algorithm is the fact that it executes at most 8 additions. The cons are that it works only for numbers that are not in two's complement. This issue is solved by saving the sign difference, storing the absolute value of the numbers, and at the end, negate the result, if there was any difference between the signs

State Diagram:

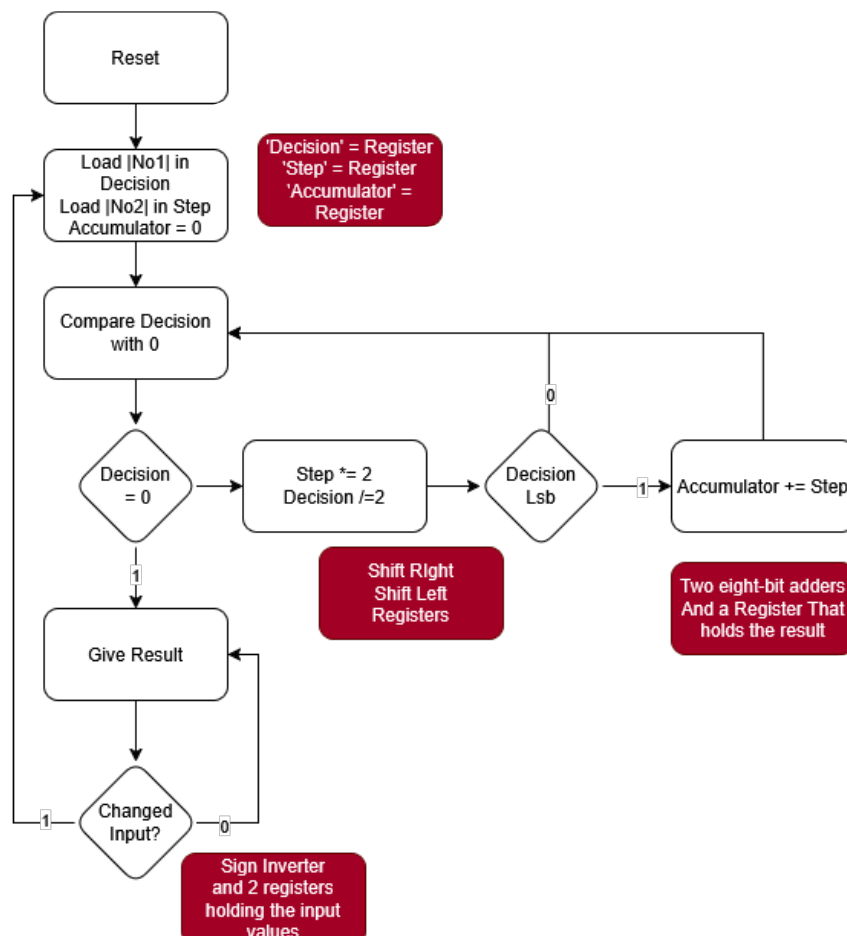



Inputs:

1. In1: first number on 8 bits
2. In2: second number on 8 bits
3. Clk : clock signal for sequential execution
4. Rst: Asynchronous reset

Outputs:

1. Multiplication result on 16 bits

Vhdl Code:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  entity multiplier_16_bit is
5      Port (
6          in1 : in  STD_LOGIC_VECTOR (7 downto 0);
7          in2 : in  STD_LOGIC_VECTOR (7 downto 0);
8          Clk : in  STD_LOGIC;
9          Rst : in  STD_LOGIC;
10         Outp : out STD_LOGIC_VECTOR (15 downto 0)
11     );
12 end multiplier_16_bit;
13 architecture Behavioral of multiplier_16_bit is
14     component full_adder_8bit is
15         Port (
16             A : in  STD_LOGIC_VECTOR (7 downto 0);
17             B : in  STD_LOGIC_VECTOR (7 downto 0);
18             Cin : in  STD_LOGIC;
19             Cout : out STD_LOGIC;
20             S : out STD_LOGIC_VECTOR (7 downto 0)
21         );
22     end component;
```


```

23 type state_type is (LOADING, COMPARE, ADD, SHOW_RESULT);
24 signal current_state: state_type := LOADING;
25 signal store_n1: STD_LOGIC_VECTOR (7 downto 0) := x"00";
26 signal store_n2 : STD_LOGIC_VECTOR (7 downto 0) := x"00";
27 signal Accumulator : STD_LOGIC_VECTOR (15 downto 0) := x"0000";
28 signal Step : STD_LOGIC_VECTOR (15 downto 0) := x"0000";
29 signal Decision : STD_LOGIC_VECTOR (7 downto 0) := x"00";
30 signal next_Accumulator: STD_LOGIC_VECTOR (15 downto 0) := x"0000";
31 signal next_Step : STD_LOGIC_VECTOR (15 downto 0) := x"0000";
32 signal next_Decision : STD_LOGIC_VECTOR (7 downto 0) := x"00";
33 signal equal_zero : STD_LOGIC := '0';
34 signal internal_carry : STD_LOGIC := '0';
35 signal different_sign : STD_LOGIC := '0';
36
37 begin
38   c1: full_adder_8bit port map (
39     A => Accumulator(7 downto 0),
40     B => Step(7 downto 0),
41     Cin => '0',
42     Cout => internal_carry,
43     S => next_Accumulator(7 downto 0)
44   );
45   c2: full_adder_8bit port map (
46     A => Accumulator(15 downto 8),
47     B => Step(15 downto 8),
48     Cin => internal_carry,
49     Cout => open,
50     S => next_Accumulator(15 downto 8)
51   );
52
53   next_Step <= Step(14 downto 0) & '0';
54   next_Decision <= '0' & Decision(7 downto 1);
55   equal_zero <= not (Decision(0) or Decision(1) or Decision(2) or
56                     Decision(3) or Decision(4) or Decision(5) or
57                     Decision(6) or Decision(7));
58
59   process(CLK, RST)
60   begin
61     if Rst = '1' then
62       current_state <= LOADING;
63       Accumulator <= x"0000";
64       Step <= x"0000";
65       Decision <= x"00";
66       store_n1 <= x"00";
67       store_n2 <= x"00";
68       different_sign <= '0';
69       Outp <= x"0000";
70     elsif rising_edge(Clk) then
71       case current_state is
72         when LOADING =>
73           Accumulator <= x"0000";
74           Step(7 downto 0) <= std_logic_vector(abs(signed(in2)));
75           Step(15 downto 8) <= x"00";
76           Decision <= std_logic_vector(abs(signed(in1)));
77           current_state <= COMPARE;
78           store_n1 <= in1;
79           store_n2 <= in2;
80           different_sign <= in1(7) xor in2(7);
81           Outp <= x"0000";
82         when COMPARE =>
83           if equal_zero = '1' then
84             current_state <= SHOW_RESULT;

```

```
83         else
84             current_state <= ADD;
85         end if;
86     when ADD =>
87         if Decision(0) = '1' then
88             Accumulator <= next_Accumulator;
89         end if;
90         Step <= next_Step;
91         Decision <= next_Decision;
92         current_state <= COMPARE;
93     when SHOW_RESULT =>
94         if ((store_n1 /= in1) or (store_n2 /= in2)) then
95             current_state <= LOADING;
96         end if;
97         if different_sign = '1' then
98             Outp <= std_logic_vector( resize((- signed( Accumulator )),16));
99         else
100             Outp <= Accumulator;
101         end if;
102     end case;
103 end if;
104 end process;
105 end Behavioral;
```

Black box representation:

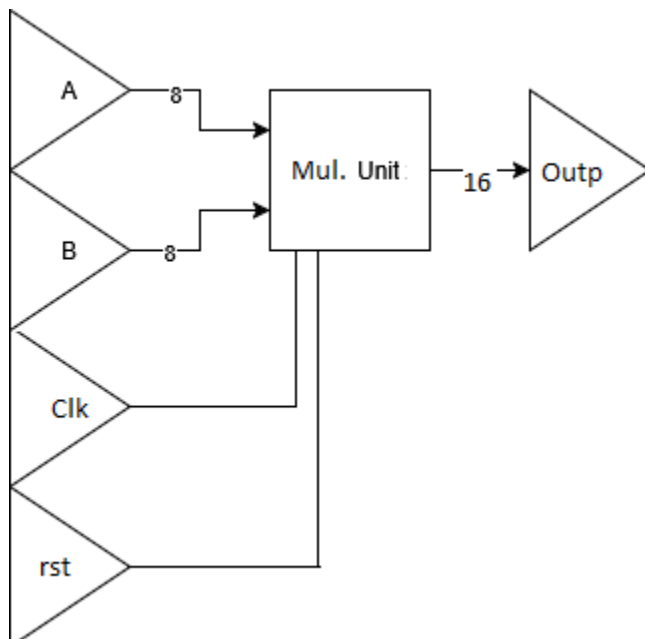


Logic representation hasn't been provided because the design is mostly behavioral, not structural, nor dataflow.

## g.Division Unit

Algorithm:

Repeated subtraction. Works for unsigned numbers. To use it for number on two's complement we just have to extract absolute value, and after the result is give, add the signe to the representation.

State Diagram:

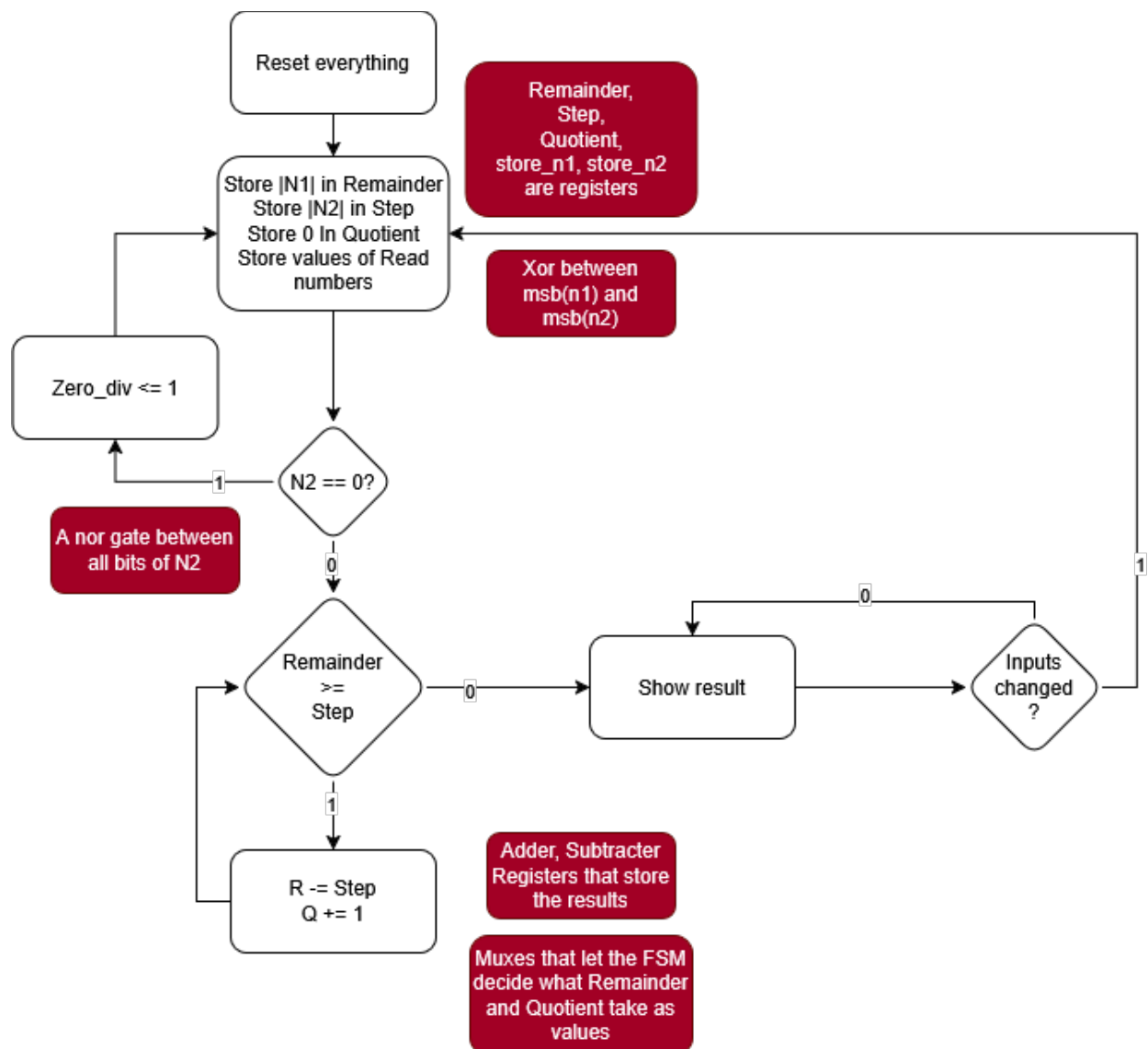

Inputs:

1. No1 : first 8bit number in 2's complement

2. No2 : second 8bit number in 2's complement
3. Clk: clock signal
4. Rst: reset signal

Outputs:

1. Quotient : modulus of quotient value
2. Remainder: modulus of remainder value
3. Sign bit : tells the output processor to put a minus sign or not in front of the quotient result
5. Zero div bit: is 1 when division by 0 takes place

Vhdl Code:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  entity division_unit is
5      Port ( nol : in STD_LOGIC_VECTOR (7 downto 0);
6            no2 : in STD_LOGIC_VECTOR (7 downto 0);
7            quotient: out std_logic_vector (7 downto 0);
8            remainder: out std_logic_vector (7 downto 0);
9            sign_bit: out std_logic;
10           zero_div: out std_logic;
11           clk : in STD_LOGIC;
12           rst : in STD_LOGIC);
13 end division_unit;
14 architecture Behavioral of division_unit is
15     component full_subtractor_8bit is
16         Port ( a : in STD_LOGIC_VECTOR (7 downto 0);
17               b : in STD_LOGIC_VECTOR (7 downto 0);
18               bin : in STD_LOGIC;
19               bout : out STD_LOGIC;
20               d : out STD_LOGIC_VECTOR (7 downto 0));
21     end component full_subtractor_8bit;
22     component full_adder_8bit is
23         Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
24               B : in STD_LOGIC_VECTOR (7 downto 0);
25               Cin : in STD_LOGIC;
26               Cout : out STD_LOGIC;
27               S : out STD_LOGIC_VECTOR (7 downto 0));
28     end component full_adder_8bit;
29     type state_type is (LOADING, COMPARE, SUBTRACT, GIVE_RESULT);
30     signal current_state: state_type := LOADING;

```


```

31 signal R : std_logic_vector ( 7 downto 0);
32 signal S : std_logic_vector ( 7 downto 0);
33 signal Q : std_logic_vector ( 7 downto 0);
34 signal bigger : std_logic;
35 signal equal : std_logic;
36 signal next_Q : std_logic_vector (7 downto 0);
37 signal next_R : std_logic_vector (7 downto 0);
38 signal no1_abs : std_logic_vector(7 downto 0);
39 signal no2_abs : std_logic_vector(7 downto 0);
40 signal store_n1 : std_logic_vector( 7 downto 0);
41 signal store_n2 : std_logic_vector( 7 downto 0);
42 signal zero : std_logic;
43 begin
44 bigger <= '1' when UNSIGNED(R) > UNSIGNED(S) else '0';
45 equal <= '1' when UNSIGNED(R) = UNSIGNED(S) else '0';
46 c1: full_subtractor_8bit port map ( a => R, b => S, bin => '0', bout => open, d=> next_R);
47 c2: full_adder_8bit port map( a => Q, b => x"00", Cin => '1', Cout => open, S => next_Q);
48 sign_bit <= no1(7) xor no2(7);
49 zero <= not ( no2(0) or no2(1) or no2(2) or
50              no2(3) or no2(4) or no2(5) or
51              no2(6) or no2(7) );
52 zero_div <= zero;
53 process(clk, rst)
54 begin
55     if rst = '1' then
56         current_state <= LOADING;
57         R <= std_logic_vector(abs(signed(no1)));
58         S <= std_logic_vector(abs(signed(no2)));
59         Q <= x"00";
60         store_n1 <= no1;
61
62         store_n2 <= no2;
63     elsif zero = '1' then
64         current_state <= LOADING;
65     elsif rising_edge(clk) then
66         case current_state is
67             when LOADING =>
68                 R <= std_logic_vector(abs(signed(no1)));
69                 S <= std_logic_vector(abs(signed(no2)));
70                 Q <= x"00";
71                 current_state <= COMPARE;
72                 store_n1 <= no1;
73                 store_n2 <= no2;
74             when COMPARE =>
75                 if (bigger = '1' or equal = '1') then
76                     current_state <= SUBTRACT;
77                 else
78                     current_state <= GIVE_RESULT;
79                 end if;
80             when SUBTRACT=>
81                 R <= next_R;
82                 Q <= next_Q;
83                 current_state <= COMPARE;
84             when GIVE_RESULT=>
85                 if store_n1 /= no1 or store_n2 /= no2 then
86                     current_state <= LOADING;
87                 end if;
88                 quotient <= Q;
89                 remainder<= R;

```

```
89   end case;  
90   end if;  
91   end process;  
92  
93   end Behavioral;  
94
```

Black box:

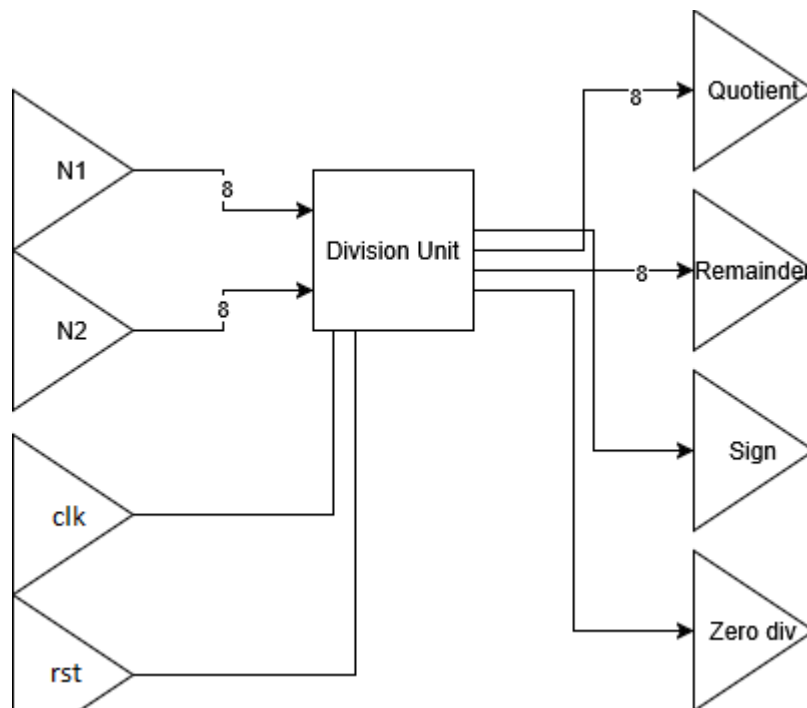

Logic representation hasn't been provided because the design is mostly behavioral, not structural, nor dataflow.

## h.Output processors

It's a collection of ROMs that have variable ranges.

Each digit of the number in base 10 has a corresponding seven-segment display value:

"C0"	0
"F9"	1
"A4"	2
"B0"	3
"99"	4
"92"	5
"82"	6
"F8"	7
"80"	8
"90"	9
"BF"	'.'
"AF"	'r'

1. Addition output processor
2. Subtraction output processor

Each number is directly converted from signed to integer and then to ROM(integer\_value).

Range is from -256 to 255.

```
outp(31 downto 0) <= ROM(to_integer(signed(inp)));  
outp(63 downto 32) <= x"C0C0C0C0";
```

3. Multiplication output processor

Same thing as above but from -32768 to 32767.

```
outp <= ROM(to_integer(signed(inp)));
```

4. Division output processor



Output is as follows:

```
sign <= x"C0" when sign_bit = '0' else x"BF";
```

```
outp(63 downto 56) <= sign;
```


```
outp(55 downto 32) <= ROM(to_integer(unsigned(quotient)));
```

```
outp(31 downto 24) <= x"AF";
```

```
outp(23 downto 0) <= ROM(to_integer(unsigned(remainder)));
```

Total source code is provided in the attached source files.

 Division display scheme on the seven segment display:



## **i. ALU general structure**

Purpose:

To calculate the 7segment result of two given input numbers in 8bits two's complement and a operation.


Inputs:

1. No1: first given number in two's complement
2. No2: second given number in two's complement
3. S: operation selection bits
4. Clk: clock signal
5. Rst : reset signal


Outputs:

1. Rez: 64 bits which represent the operation and input's result in 7 segment encoding

Logic Scheme:

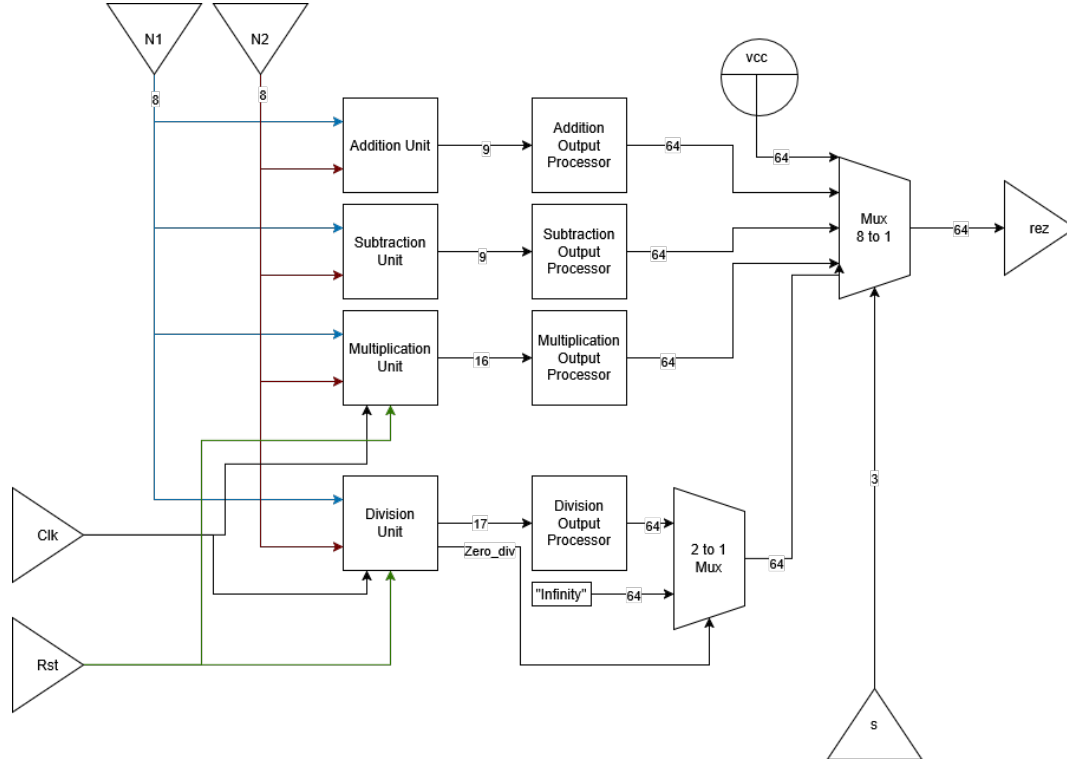

Black box:

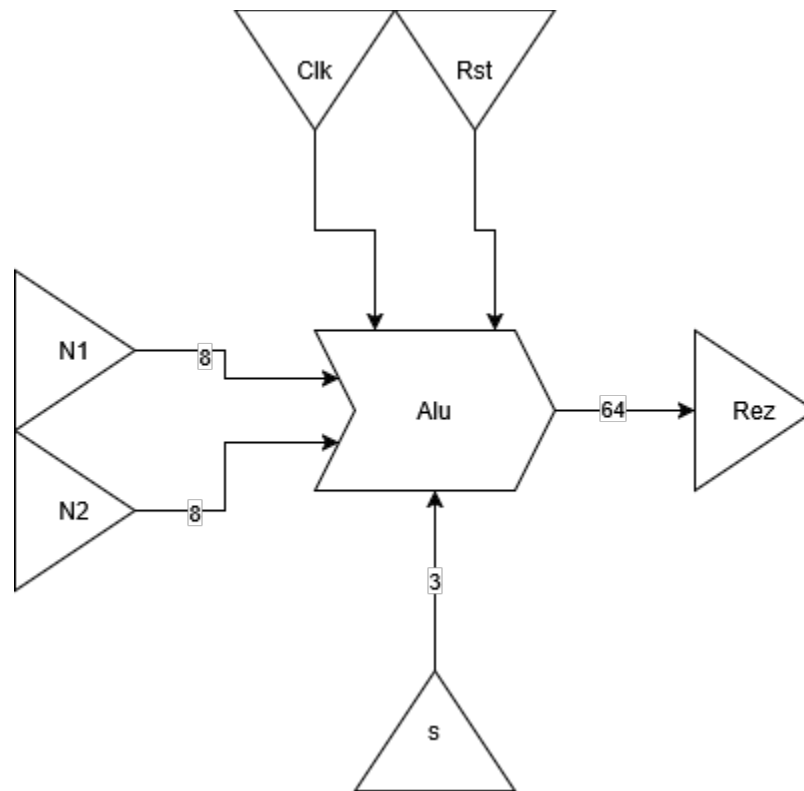

## Vhdl Code:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  entity arithmetic_logic_unit is
5      Port ( no1 : in STD_LOGIC_VECTOR (7 downto 0);
6            no2 : in STD_LOGIC_VECTOR (7 downto 0);
7            s : in STD_LOGIC_VECTOR (2 downto 0);
8            clk : in std_logic;
9            rst : in std_logic;
10           rez : out STD_LOGIC_VECTOR (63 downto 0));
11 end arithmetic_logic_unit;
12 architecture Behavioral of arithmetic_logic_unit is
13 component multiplier_16_bit is
14     Port ( in1 : in STD_LOGIC_VECTOR (7 downto 0);
15           in2 : in STD_LOGIC_VECTOR (7 downto 0);
16           Clk : in STD_LOGIC;
17           Rst : in STD_LOGIC;
18           Outp : out STD_LOGIC_VECTOR (15 downto 0));
19 end component multiplier_16_bit;
20 component multiplication_output_processor is
21     Port (
22         inp : in std_logic_vector (15 downto 0);
23         outp: out std_logic_vector(63 downto 0)
24     );
25 end component multiplication_output_processor;

26 component division_unit is
27     Port ( no1 : in STD_LOGIC_VECTOR (7 downto 0);
28           no2 : in STD_LOGIC_VECTOR (7 downto 0);
29           quotient: out std_logic_vector (7 downto 0);
30           remainder: out std_logic_vector (7 downto 0);
31           sign_bit: out std_logic;
32           zero_div: out std_logic;
33           clk : in STD_LOGIC;
34           rst : in STD_LOGIC);
35 end component division_unit;
36 component division_output_processor is
37     Port (
38         quotient: in std_logic_vector (7 downto 0);
39         remainder: in std_logic_vector (7 downto 0);
40         sign_bit: in std_logic;
41         outp : out std_logic_vector (63 downto 0));
42 end component division_output_processor;
43 component adder_unit is
44     Port (
45         A : in STD_LOGIC_VECTOR (7 downto 0);
46         B : in STD_LOGIC_VECTOR (7 downto 0);
47         S : out STD_LOGIC_VECTOR (8 downto 0)
48     );
49 end component adder_unit;
50 component addition_output_processor is
51     Port(
52         inp : in std_logic_vector ( 8 downto 0);
53         outp: out std_logic_vector( 63 downto 0)
54     );
55 end component addition_output_processor;

```




```
115 c2: adder_unit port map (A => no1, B => no2, S => add_final);
116 c3: subtracter_unit port map (A => no1, B => no2, D => Sub_final);
117 c4: multiplier_16_bit port map ( in1 => no1, in2 => no2,
118                               Clk=> clk, Rst=> rst, Outp => mul);
119 c5: division_unit port map ( no1 => no1, no2 => no2, quotient => div(15 downto 8),
120                             remainder => div(7 downto 0), sign_bit=>sign_bit,
121                             zero_div => zero_div, clk=> clk, rst=>rst);
122 c6: addition_output_processor port map (inp => add_final, outp => add_rez_string);
123 c7: subtraction_output_processor port map ( inp => sub_final, outp => sub_rez_string);
124 c8: division_output_processor port map ( quotient => div ( 15 downto 8),
125                                         remainder=> div ( 7 downto 0),
126                                         sign_bit => sign_bit,
127                                         outp=> div_rez_string);
128 c9: multiplication_output_processor port map( inp => mul, outp => mul_rez_string);
129 end Behavioral;
130
```

### 3. Display Unit

#### a. Eight-bit two's complement to seven segment display ROM

Same logic as the "Output Processor". Takes in a number in 8-bit 2's complement and outputs the corresponding bitstring.

Black box:

 

#### b. Three-bit counter with clock divider

Purpose:

To alter between digits and allow the seven-segment display. Takes in the clock signal and every 100000 clock cycles goes to the next state (0 to 7)

Inputs:


1. Clk: clock signal
2. Rst: reset signal

Outputs:


1. Outp : 3-bit signal which signals the state to the 7 segment displayer.



Logic Scheme:

 

Black-box:

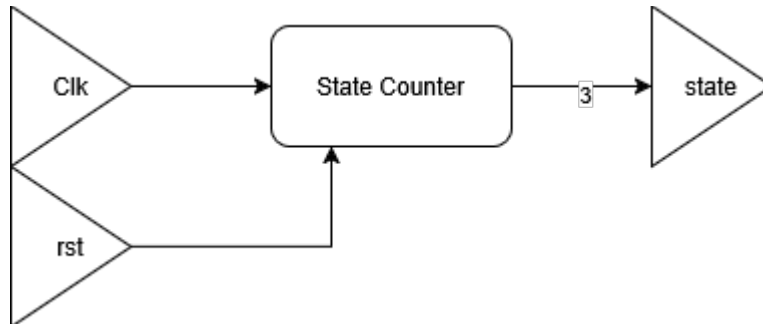

VHDL Code:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  entity three_bit_counter is
5      Port (
6          clk: in STD_LOGIC;
7          rst: in STD_LOGIC;
8          outp : out STD_LOGIC_VECTOR (2 downto 0));
9  end three_bit_counter;
10 architecture Behavioral of three_bit_counter is
11     signal state: unsigned(2 downto 0) := "000";
12     signal counter : unsigned(16 downto 0) := (others => '0');
13     constant divider: integer := 1000000;
14 begin
15     outp <= std_logic_vector(state);
16     process(clk, rst)
17     begin
18         if rst = '1' then
19             state <= "000";
20             counter <= (others => '0');
21         elsif rising_edge(clk) then
22             if counter = divider - 1 then
23                 counter <= (others => '0');
24                 state <= state + 1;
25             else
26                 counter <= counter + 1;
27             end if;
28         end if;
29     end process;
30 end Behavioral;

```

## c.Seven segment displayer

### i. Three-bit decoder


Purpose:

To tell the Seven-segment display what digit position to display the selected digit onto.


Inputs: Inp : 3 bits

Outputs: Outp: 8 bits, active-low when corresponding combination is inserted.

Logic scheme:

 

Black box:

 

VHDL Code:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  entity decoder_3_bit is
5      Port ( inp : in STD_LOGIC_VECTOR (2 downto 0);
6            outp : out STD_LOGIC_VECTOR (7 downto 0));
7  end decoder_3_bit;
8
9  architecture Behavioral of decoder_3_bit is
10
11      begin
12
13          outp(0) <= '0' when inp = "000" else '1';
14          outp(1) <= '0' when inp = "001" else '1';
15          outp(2) <= '0' when inp = "010" else '1';
16          outp(3) <= '0' when inp = "011" else '1';
17          outp(4) <= '0' when inp = "100" else '1';
18          outp(5) <= '0' when inp = "101" else '1';
19          outp(6) <= '0' when inp = "110" else '1';
20          outp(7) <= '0' when inp = "111" else '1';
21
22      end Behavioral;
    
```

## ii. 8 to 1 Mux on 8 bits

Purpose :

Breaks down the 64-bit 7-segment info into separate digits for 'on-screen' writing

Inputs:

1. Inp : the 64 bits that represent the choices
2. S : 3 bits that represent the choice bits


Outputs:

1. Outp: the selected 8 bits

VHDL code:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  entity mux_8to1_8bit is
5      Port ( inp : in STD_LOGIC_VECTOR (63 downto 0);
6            s : in STD_LOGIC_VECTOR (2 downto 0);
7            outp : out STD_LOGIC_VECTOR (7 downto 0));
8  end mux_8to1_8bit;
9  architecture Behavioral of mux_8to1_8bit is
10 begin
11     outp <= inp(7 downto 0)   when s = "000" else
12             inp(15 downto 8)  when s = "001" else
13             inp(23 downto 16) when s = "010" else
14             inp(31 downto 24) when s = "011" else
15             inp(39 downto 32) when s = "100" else
16             inp(47 downto 40) when s = "101" else
17             inp(55 downto 48) when s = "110" else
18             inp(63 downto 56) when s = "111";
19 end Behavioral;
```

Black box:

 

### iii. Seven Segment Displayer General Structure

Purpose:

To select and transfer the given 7-segment information required to be displayed.


Inputs:

1. Info : the total 64-string to be displayed on the 7-segment display
2. State: 3-bits which decide the output


Outputs:

1. Digit\_info : that's the multiplexed digit info
2. Anodes : what's the chosen digit to write to

Logic Scheme:

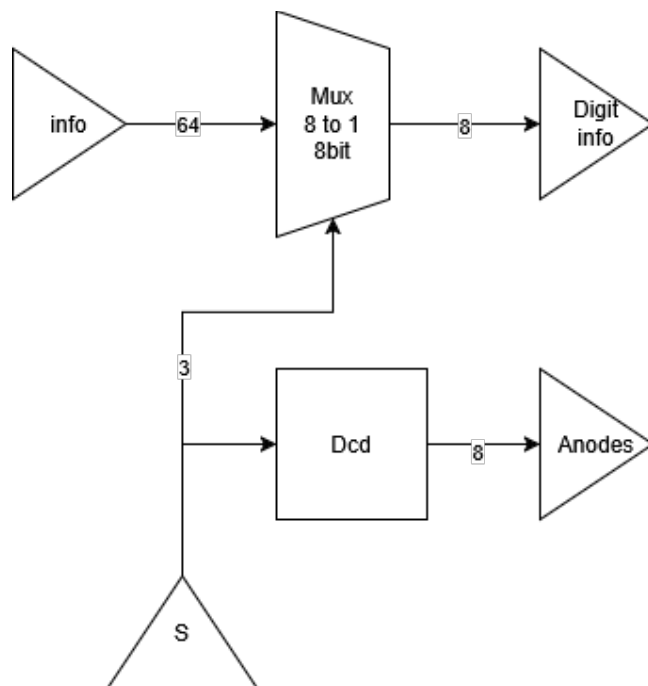

Black box:

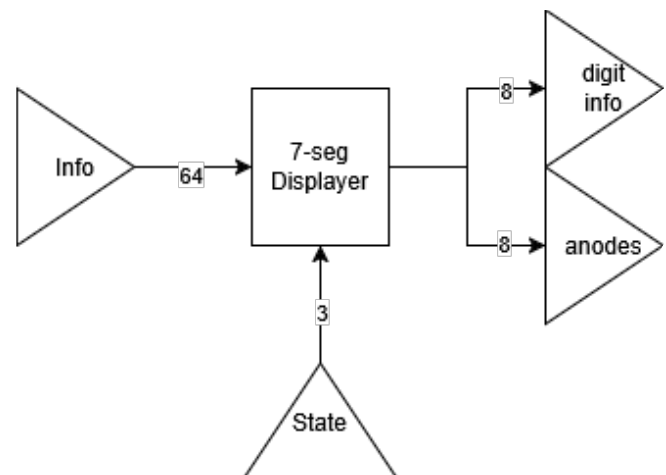

## Vhdl Code:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  entity seven_seg_displayer is
5      Port ( info : in STD_LOGIC_VECTOR (63 downto 0);
6            state : in STD_LOGIC_VECTOR (2 downto 0);
7            digit_info : out STD_LOGIC_VECTOR (7 downto 0);
8            anodes : out STD_LOGIC_VECTOR (7 downto 0));
9  end seven_seg_displayer;
10
11  architecture Behavioral of seven_seg_displayer is
12
13  component mux_8tol_8bit is
14      Port ( inp : in STD_LOGIC_VECTOR (63 downto 0);
15            s : in STD_LOGIC_VECTOR (2 downto 0);
16            outp : out STD_LOGIC_VECTOR (7 downto 0));
17  end component mux_8tol_8bit;
18
19  component decoder_3_bit is
20      Port ( inp : in STD_LOGIC_VECTOR (2 downto 0);
21            outp : out STD_LOGIC_VECTOR (7 downto 0));
22  end component decoder_3_bit;
23
24  begin
25  c0: decoder_3_bit port map (inp => state, outp => anodes);
26  c1: mux_8tol_8bit port map ( inp => info, s => state, outp => digit_info);
27  end Behavioral;
28
```

## d. Display Unit general Structure

Purpose:


To take the input numbers and the ALU Result and show those on the 7-segment display.

Inputs:

1. No1 : the first inserted 8-bit 2's complement number
2. No2 : the second inserted 8-bit 2's complement number
3. Rez : the ALU result
4. Clk : clock signal
5. Rst: reset signal
6. S : picks between displaying input numbers and result


Outputs:

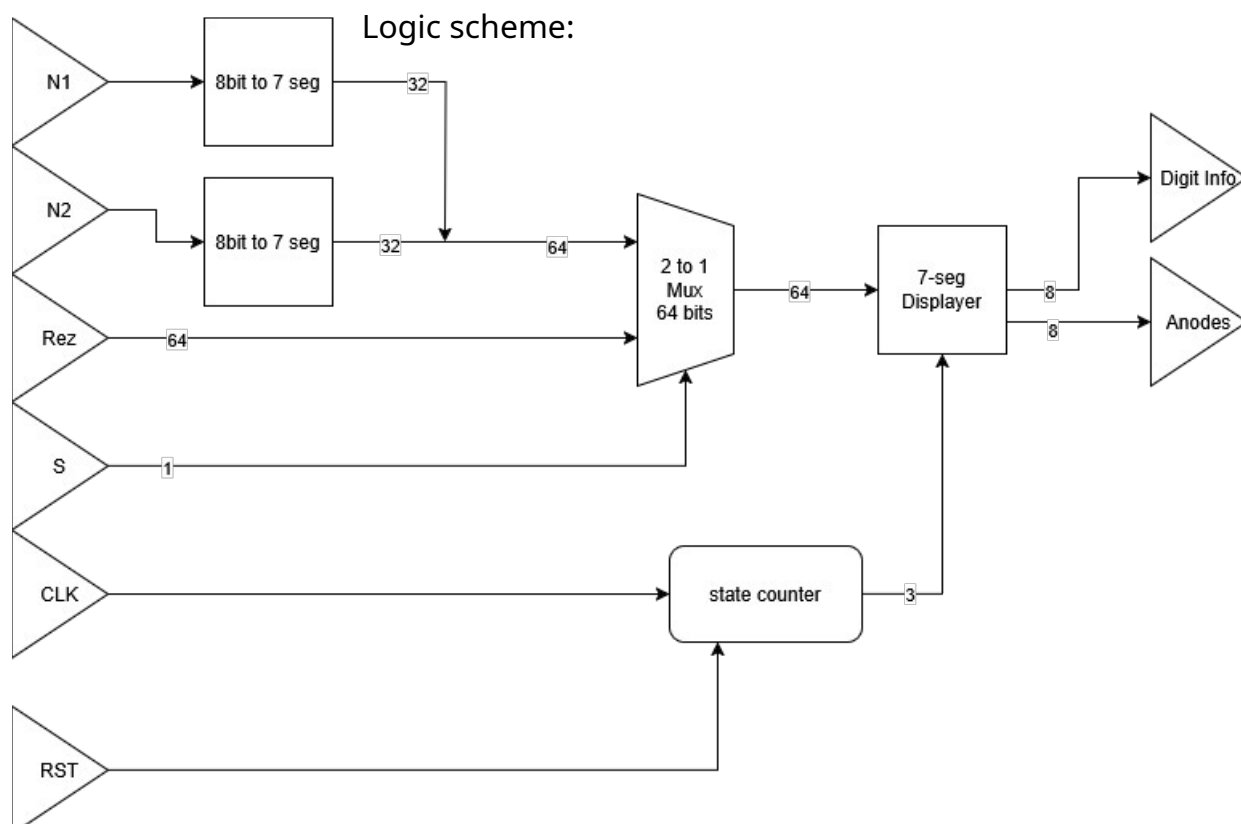1. Digit\_info : the 7-segment information which chooses which segment lights up
2. Anode\_info : 8-bits which pick the target 7-segment digit





Black box:

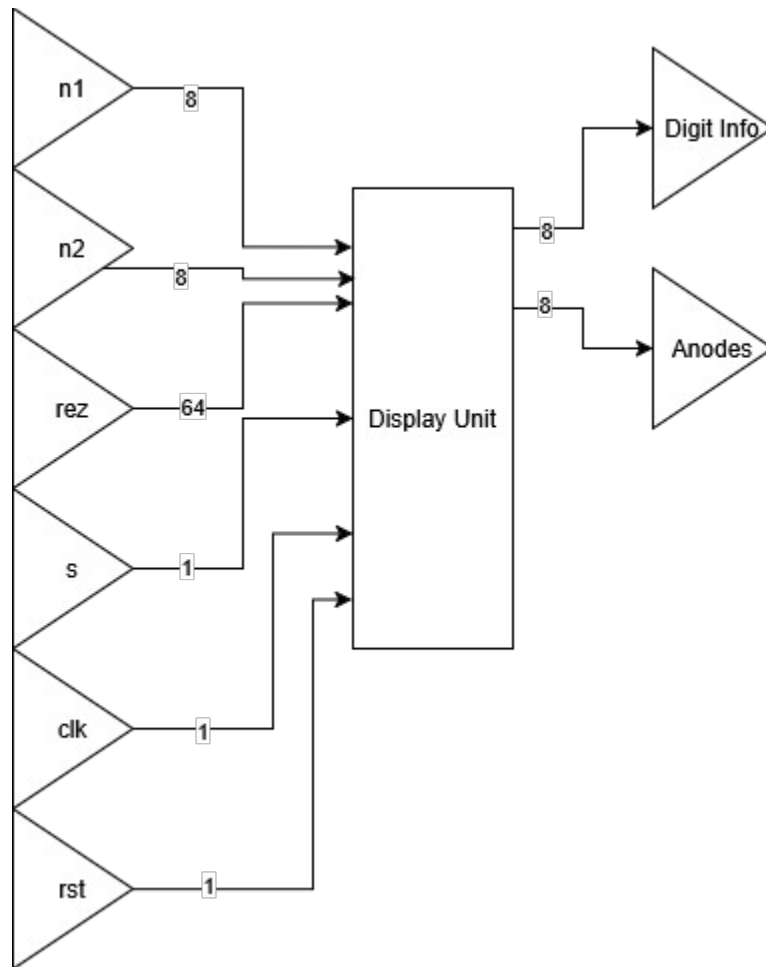

VHDL Code:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity display_unit is
6      Port ( n01 : in STD_LOGIC_VECTOR (7 downto 0);
7            n02 : in STD_LOGIC_VECTOR (7 downto 0);
8            rez : in STD_LOGIC_VECTOR (63 downto 0);
9            s   : in STD_LOGIC;
10           clk : in STD_LOGIC;
11           rst : in STD_LOGIC;
12           digit_info : out STD_LOGIC_VECTOR (7 downto 0);
13           anode_info : out STD_LOGIC_VECTOR (7 downto 0));
14 end display_unit;

```

```

15
16 architecture Behavioral of display_unit is
17 component Eight_bit_twos_complement_to_seven_seg_display is
18     Port ( number : in STD_LOGIC_VECTOR (7 downto 0);
19           display : out STD_LOGIC_VECTOR (31 downto 0));
20 end component Eight_bit_twos_complement_to_seven_seg_display;
21 component mux_2tol_64bits is
22     Port ( in1 : in STD_LOGIC_VECTOR (63 downto 0);
23           in2 : in STD_LOGIC_VECTOR (63 downto 0);
24           s : in STD_LOGIC;
25           outp : out STD_LOGIC_VECTOR (63 downto 0));
26 end component mux_2tol_64bits;
27 component three_bit_counter is
28     Port ( clk : in STD_LOGIC;
29           rst : in STD_LOGIC;
30           outp : out STD_LOGIC_VECTOR (2 downto 0));
31 end component three_bit_counter;
32 component seven_seg_displayer is
33     Port ( info : in STD_LOGIC_VECTOR (63 downto 0);
34           state : in STD_LOGIC_VECTOR (2 downto 0);
35           digit_info : out STD_LOGIC_VECTOR (7 downto 0);
36           anodes : out STD_LOGIC_VECTOR (7 downto 0));
37 end component seven_seg_displayer;
38 signal rn1_concat_rn2 : std_logic_vector (63 downto 0);
39 signal n1 : STD_LOGIC_VECTOR (7 downto 0);
40 signal n2 : STD_LOGIC_VECTOR (7 downto 0);
41 signal decision : std_logic_vector (63 downto 0);
42 signal state_cnt : std_logic_vector (2 downto 0);
43 begin
44
45 begin
46 n1 <= n01;
47 n2 <= n02;
48
49 c0: Eight_bit_twos_complement_to_seven_seg_display port map ( number => n1,
50                                                                display => rn1_concat_rn2 (63 downto 32));
51 c1: Eight_bit_twos_complement_to_seven_seg_display port map ( number => n2,
52                                                                display => rn1_concat_rn2 (31 downto 0));
53 c3: mux_2tol_64bits port map ( in1 => rez , in2 => rn1_concat_rn2 ,
54                               s => s, outp => decision);
55 c4: three_bit_counter port map ( clk => clk, rst => rst, outp => state_cnt);
56 c7: seven_seg_displayer port map ( info => decision, state => state_cnt,
57                                   digit_info => digit_info, anodes => anode_info);
58 end Behavioral;

```

## 4.Execution Unit General Structure

Purpose:

To execute all computation required by the control unit.


Inputs:

1. N1: first input number in 8bits two's complement
2. N2 : second input number in 8bits two's complement
3. S : three bit choice signal

Outputs:

1. Digit\_info : same as Display Unit
2. Anode\_info: same as Display Unit

Logic scheme:

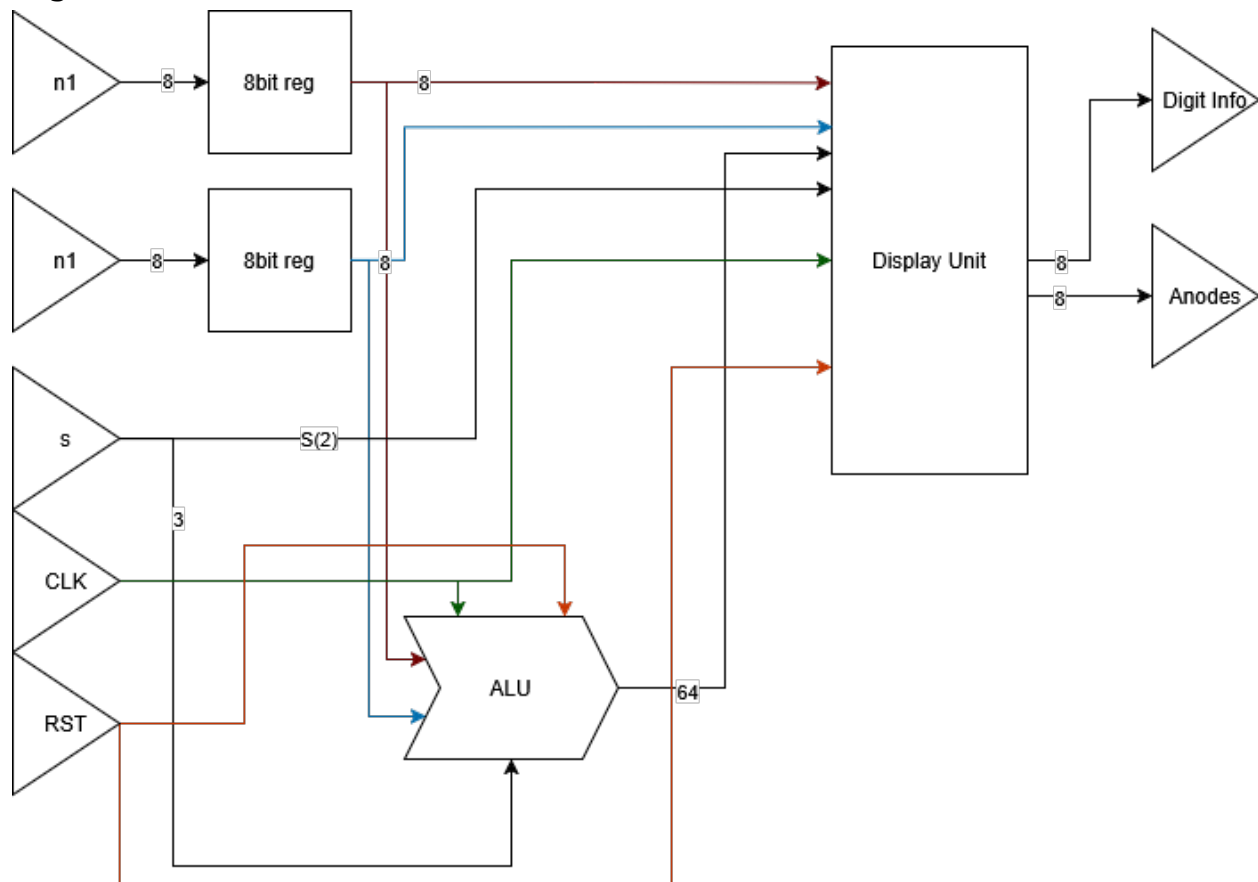

Black Box : (Shown above in component block diagram)

Vhdl Code:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  entity Execution_Unit is
4      Port (
5          n1 : in std_logic_vector ( 7 downto 0);
6          n2 : in std_logic_vector ( 7 downto 0);
7          s  : in std_logic_vector ( 2 downto 0);
8          clk: in std_logic;
9          rst: in std_logic;
10         digit_info : out STD_LOGIC_VECTOR (7 downto 0);
11         anode_info  : out STD_LOGIC_VECTOR (7 downto 0));
12 end Execution_Unit;
13 architecture Behavioral of Execution_Unit is
14     component display_unit is
15         Port ( no1 : in STD_LOGIC_VECTOR (7 downto 0);
16               no2 : in STD_LOGIC_VECTOR (7 downto 0);
17               rez : in STD_LOGIC_VECTOR (63 downto 0);
18               s   : in STD_LOGIC;
19               clk  : in STD_LOGIC;
20               rst  : in STD_LOGIC;
21               digit_info : out STD_LOGIC_VECTOR (7 downto 0);
22               anode_info : out STD_LOGIC_VECTOR (7 downto 0));
23     end component display_unit;
24     component arithmetic_logic_unit is
25         Port ( no1 : in STD_LOGIC_VECTOR (7 downto 0);
26               no2 : in STD_LOGIC_VECTOR (7 downto 0);
27               s   : in STD_LOGIC_VECTOR (2 downto 0);
28               clk  : in std_logic;
29               rst  : in std_logic;
30               rez  : out STD_LOGIC_VECTOR (63 downto 0));
31     end component arithmetic_logic_unit;
32     component data_register_8_bit is
33         Port ( Load : in STD_LOGIC;
34               Clk   : in STD_LOGIC;
35               Rst   : in STD_LOGIC;
36               Load_inp : in STD_LOGIC_VECTOR (7 downto 0);
37               Outp   : out STD_LOGIC_VECTOR (7 downto 0));
38     end component data_register_8_bit;
39     signal no1_stored : std_logic_vector ( 7 downto 0);
40     signal no2_stored : std_logic_vector ( 7 downto 0);
41     signal rez        : std_logic_vector ( 63 downto 0);
42     begin
43         c0: data_register_8_bit port map ( Load => s(2), Clk => clk,
44                                           Rst => rst, Load_inp => n1, outp => no1_stored);
45         c1: data_register_8_bit port map ( Load => s(2), Clk => clk,
46                                           Rst => rst, Load_inp => n2, outp => no2_stored);
47         c2: arithmetic_logic_unit port map ( no1 => no1_stored, no2 => no2_stored,
48                                             s => s, clk=>clk, rst => rst, rez => rez);
49         c3: display_unit port map ( no1 => no1_stored, no2 => no2_stored, rez => rez, s => s(2),
50                                   clk => clk, rst => rst, digit_info => digit_info, anode_info => anode_info);
51     end Behavioral;
52

```

## Control unit

### Button Push Decoder Logic

Here is the decoder logic for the button pushes

Add Button	Subtraction Button	Multiplication Button	Division Button	Result
1	0	0	0	000
0	1	0	0	001
0	0	1	0	010
0	0	0	1	011
Other cases	Other cases	Other Cases	Other Cases	100

“Result” is directly sent as ‘s’ towards the execution unit.

Purpose:

To control the operation of the whole project.

Inputs / Outputs / Black box: Exemplified in the Component block diagram

VHDL Code:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  entity Control_Unit is
4      Port ( N1 : in STD_LOGIC_VECTOR (7 downto 0);--
5            N2 : in STD_LOGIC_VECTOR (7 downto 0);--
6            Add_button : in STD_LOGIC;
7            Sub_button : in STD_LOGIC;
8            Mul_button : in STD_LOGIC;
9            Div_button : in STD_LOGIC;
10           Rst_button : in STD_LOGIC;
11           Clk : in STD_LOGIC;
12           N1_eu : out STD_LOGIC_VECTOR (7 downto 0);
13           N2_eu : out STD_LOGIC_VECTOR (7 downto 0);
14           restart_eu : out std_logic;
15           OP : out STD_LOGIC_VECTOR (2 downto 0);
16           seven_seg_eu : in STD_LOGIC_VECTOR (15 downto 0);
17           seven_seg : out STD_LOGIC_VECTOR (15 downto 0));
18  end Control_Unit;
19  architecture Behavioral of Control_Unit is
20      type state_type is ( RESET, WAIT_OP, ADD, SUB, MUL, DIV);
21      signal current_state : state_type := RESET;
22      signal operation : std_logic_vector (2 downto 0) := "100";
23  begin

30      if rising_edge(clk) then
31          restart_eu <= '0';
32          case current_state is
33              when RESET =>
34                  operation <= "100";
35                  restart_eu <= '1';
36                  current_state <= WAIT_OP;
37              when WAIT_OP =>
38                  operation <= "100";
39                  if Add_button = '1' then
40                      current_state <= ADD;
41                  elsif sub_button = '1' then
42                      current_state <= SUB;
43                  elsif mul_button = '1' then
44                      current_state <= MUL;
45                  elsif div_button = '1' then
46                      current_state <= DIV;
47                  elsif rst_button = '1' then
48                      current_state <= RESET;
49                  end if;
50              when ADD =>
51                  operation <= "000";
52                  if rst_button = '1' then
53                      current_state <= RESET;
54                  end if;
55          end case;
56      end if;
```

```
55 when SUB =>  
56     operation <= "001";  
57     if rst_button = '1' then  
58         current_state <= RESET;  
59     end if;  
60 when MUL =>  
61     operation <= "010";  
62     if rst_button = '1' then  
63         current_state <= RESET;  
64     end if;  
65 when DIV =>  
66     operation <= "011";  
67     if rst_button = '1' then  
68         current_state <= RESET;  
69     end if;  
70 end case;  
71 end if;  
72 end process;  
73  
74 end Behavioral;  
75
```

State Diagram: Has been shown in the introduction.